

# PREVIOUS STUDY SESSION 4

## Sonia Navas Rutete & Jorge Rodrigo Leclercq


### EXERCISE 1

As the period is  $T = 1/f = 1/1 = 1s$ , that means that in each rising edge of clk we will have 1 second, so we need 5 cycles to get 5 seconds( =5 rising-edges). So the maximum value for count will be 100 in binary(if we count the 000).
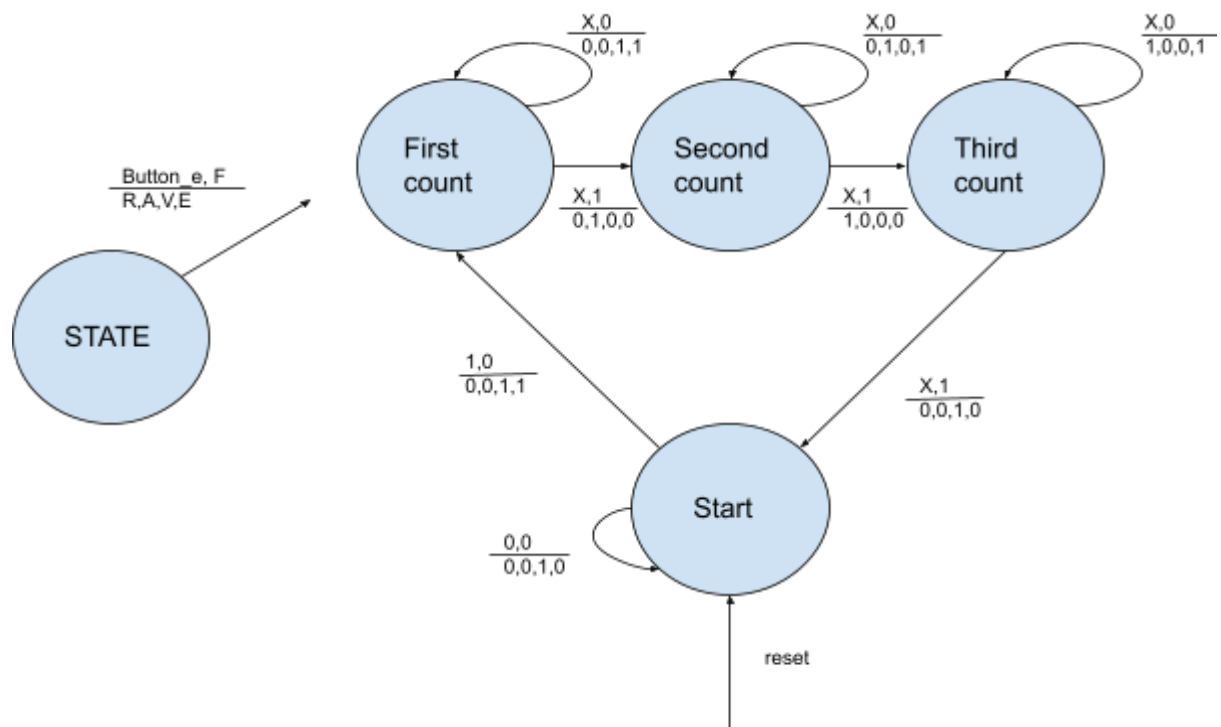
### EXERCISE 2

We have chosen a mealy machine as the output is affected by the state and the input.

As the button is only used in the start state, in the rest of situations it doesn't matter (button: x). In addition The enable will always be 1 and change to 0 automatically, to reset the count.





```
        else
            next_state <= second;
        end if;
    when second =>
        RAG <= "010";
        if f = '0' then
            next_state <= current_state;
        else
            next_state <= third;
        end if;
    when third =>
        RAG <= "100";
        if f = '0' then
            next_state <= current_state;
        else
            next_state <= start;
        end if;
    end case;
end process fsm;
end functional;
```